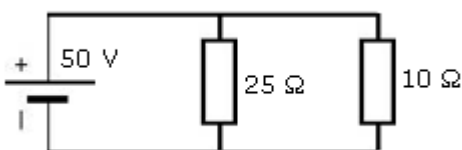


BASIC ELECTRICAL CIRCUITS


ELECTRICITY EXERCISES

1. We have connected a $15\text{K}\Omega$ resistor to a 60V power source. Calculate the intensity value
2. If an intensity of 50mA passes through a resistance of $2\text{K}\Omega$, what is the value of the voltage?
3. Three resistors $R_1=20\Omega$, $R_2=40\Omega$ and $R_3=40\Omega$ are connected in series. If the potential difference across resistor R_1 is 50V , what is the battery voltage?
4. We connect 4 resistors in series to a 24V battery. The value of the three resistors is known, they are all $4\text{K}\Omega$. We have measured the voltage drop in such a resistor and the value is 4V . Calculate the value of the fourth resistor.
5. We have 3 resistors connected in parallel: $R_1=20\Omega$, $R_2=40\Omega$ and $R_3=40\Omega$. The current flowing through R_1 is 6A . Calculate the equivalent resistance and the value of the intensity provided by the battery.
6. We connected two resistors $R_1=400\Omega$ and R_2 in parallel. The intensity provided by the battery is 1A and the intensity passing through R_1 is 600mA . Calculate the value of R_2 .
7. Calculate:
 - The intensity of the current flowing through each resistor
 - Equivalent resistance (R_B)



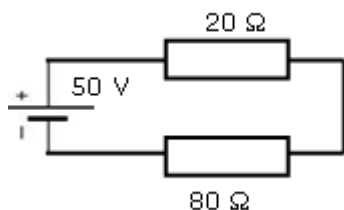
8. Calculate:

The voltage drop experienced by each resistance
Equivalent resistance (R_B)



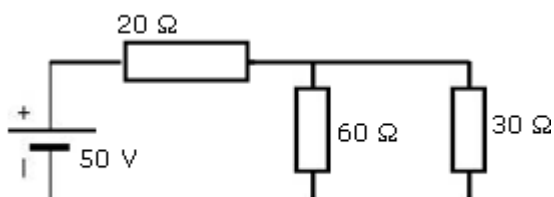
9. Calculate:

The intensity of the current flowing through each resistor
The voltage drop experienced by each resistor
Equivalent resistance (R_B)




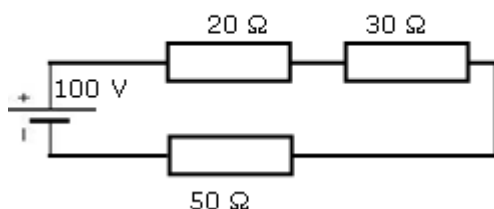10. Calculate:

The voltage drop experienced by each resistance
Equivalent resistance (R_B)




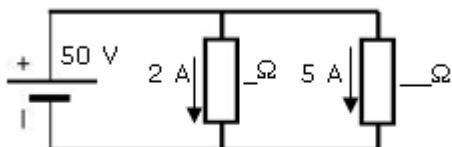11. Calculate:
 The value of each resistor




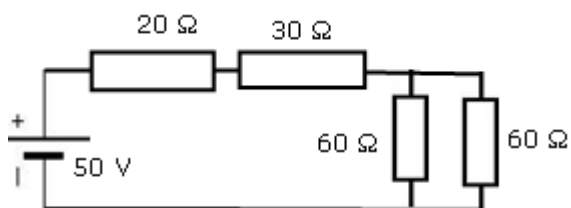12. Calculate:


- The intensity of the current flowing through each resistor
- The voltage drop experienced by each resistor
- Equivalent resistance (R_B)



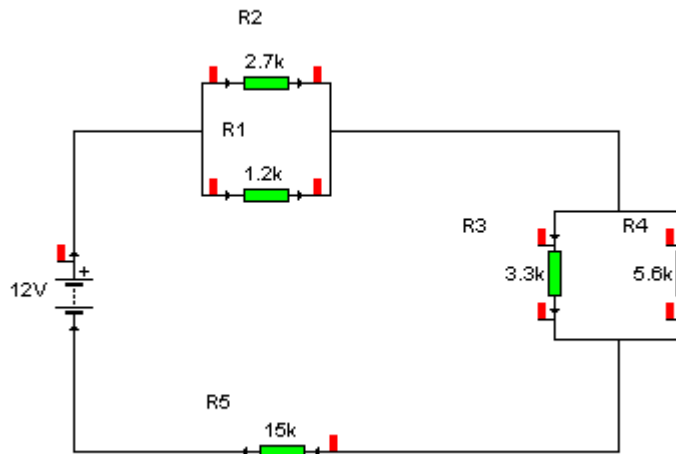13. Calculate the voltage drop across resistors R3 and R4




14. Calculate the power absorbed by R4

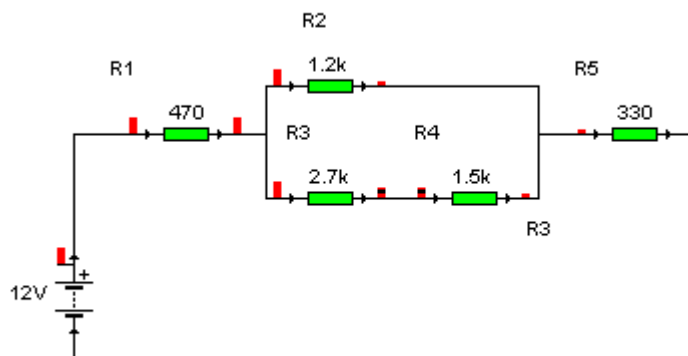


15. Calculate the following circuits:

- a) Equivalent resistance
- b) All the intensities that can be found in the circuit
- c) Voltage drops in each resistor


1. CIRCUIT:

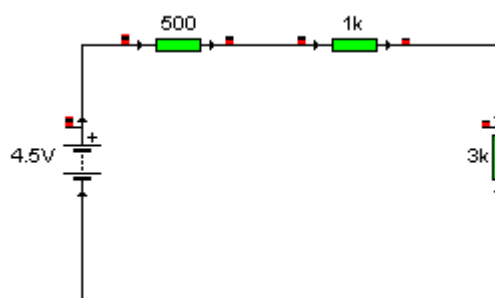

CIRCUIT 2:

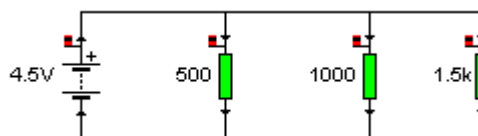


3. CIRCUIT:

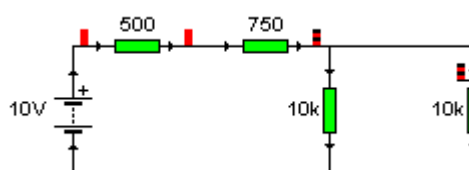

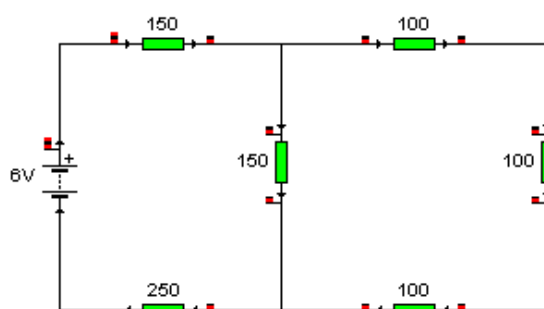
16. Calculate them in the circuit shown below:

- Equivalent resistance
- All the intensities that can be found in the circuit
- Voltage drops in each resistor
- Power dissipated in each resistor



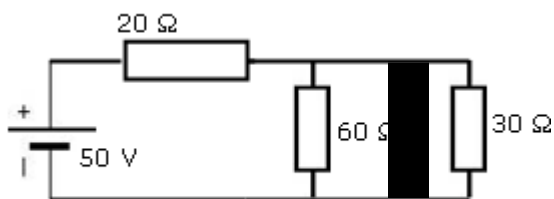
17. Calculate:

The intensity of the current flowing through each resistor
 The voltage drop experienced by each resistor
 Equivalent resistance (R_B)



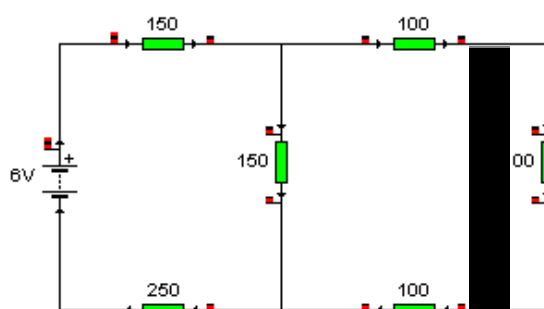
18. Calculate them in the circuit shown below:

- Equivalent resistance
- All the intensities that can be found in the circuit
- Voltage drops in each resistor
- Power dissipated in each resistor



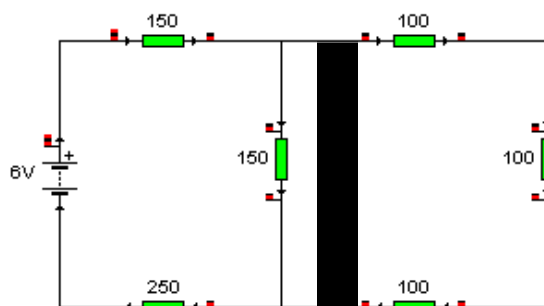19. Calculate them in the circuit shown below:


- Equivalent resistance
- All the intensities that can be found in the circuit
- Voltage drops in each resistor
- Power dissipated in each resistor




20. Calculate the following circuits:

- a) Equivalent resistance
- b) All the intensities that can be found in the circuit
- c) Voltage drops in each resistor


1. CIRCUIT:

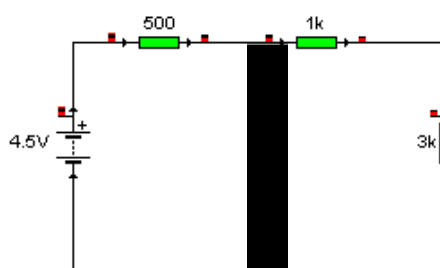

2. CIRCUIT:

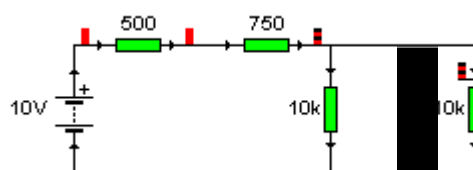

3. CIRCUIT

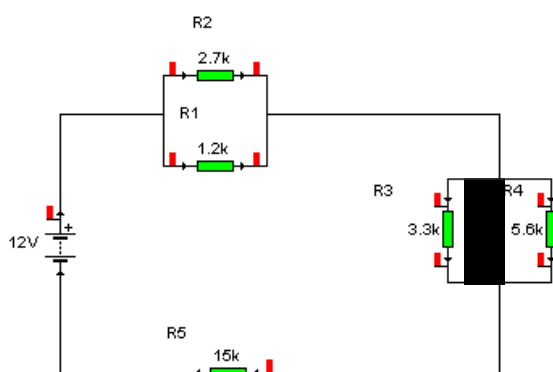

21. Calculate the power absorbed by R4

